

Supplementary Problems 2: Circuits and Capacitors

1. The quantity of charge, q , that has passed through any cross-section of a certain conductor in the time interval 0 sec. to t sec. is given by the equation

$$q(t) = 4t^3 + 5t + 6$$

where q is in coulombs.

- (a) What is the average current through the conductor from $t = 2$ s to $t = 4$ s?

Since current is defined as $I = \frac{dQ}{dt}$, the average current over a time interval will be

$I = \frac{\Delta Q}{\Delta t}$. Plugging in the equation for $q(t)$,

$$I_{ave} = \frac{Q(4) - Q(2)}{4 - 2} = \frac{1}{2}[(4 \cdot 4^3 + 5 \cdot 4 + 6) - (4 \cdot 2^3 + 5 \cdot 2 + 6)] = 117 \text{ A}$$


- (b) If the resistance of the conductor is 12Ω , what is the rate at which it is absorbing electrical energy at $t = 2$ s?

$$I = \frac{dQ}{dt} = 12t^2 + 5$$

$$I(t = 2s) = 12 \cdot 2^2 + 5 = 53 \text{ A}$$

$$P = I^2 R = 53^2 \cdot 12 = 3.37 \times 10^4 \text{ W}$$

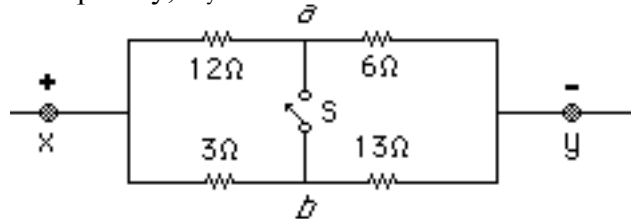2. The figure below shows a section of a circuit where the electric potential at the point x, $V_x = 64.0$ volts and at the point y, $V_y = 16.0$ volts.



- (a) With the switch S open determine the current in the 6Ω resistor **and** the potential difference V_{ab} .

With the switch open we have two parallel branches, the top with the 12Ω and 6Ω resistors in series and the bottom with the 3Ω and 13Ω resistors in series.

The potential difference across both branches is $V_{xy} = 64.0 - 16.0 = 48.0 \text{ V}$.

The equivalent resistance of the top branch is $R_{top} = 12 + 6 = 18\Omega$.

The current through the top branch, and so the 6Ω resistor, is $I_{top} = \frac{V}{R} = \frac{48.0}{18} = 2.67 \text{ A}$

The potential at a can be found by starting at either end: $V_x - V_{12\Omega}$ or $V_y + V_{6\Omega}$.

Either way, $V_a = 64 - 2.67 \cdot 12 = 16 + 2.67 \cdot 6 = 32 \text{ V}$

To find the potential at b, we also need to find the current in the bottom branch with equivalent resistance $R_{bottom} = 3 + 13 = 16\Omega$. This is $I_{bottom} = \frac{V}{R} = \frac{48}{16} = 3 \text{ A}$.

Like above, $V_b = V_x - V_{3\Omega} = V_y + V_{13\Omega} = 64 - 3 \cdot 3 = 16 + 3 \cdot 13 = 55 \text{ V}$

The potential difference is $V_a - V_b = 32 - 55 = -23 \text{ V}$

- (b) With the switch S closed determine the current through the switch (include direction) **and** V_{ab} .

With the switch closed, we now have two segments in series. On the left the 12Ω and 3Ω resistors are connected in parallel, and on the right the 6Ω and 13Ω resistors are connected in parallel.

Points a and b are now connected by an empty wire with no resistance, so $V_{ab} = 0 \text{ V}$!

To find the current through the switch, we need to first find the equivalent resistance of the entire circuit:

$$R_{left} = \left(\frac{1}{12} + \frac{1}{3} \right)^{-1} = 2.4 \Omega$$

$$R_{right} = \left(\frac{1}{6} + \frac{1}{13} \right)^{-1} = 4.1 \Omega$$

$$R_{eq} = 2.4 + 4.1 = 6.5 \Omega$$

$$I_{tot} = \frac{V_{tot}}{R_{eq}} = \frac{48.0}{6.5} = 7.38 \text{ A}$$

We can now find the voltage drop in each segment of the circuit, and then the current through each resistor.

$$V_{left} = I_{tot} R_{left} = 7.38 \cdot 2.4 = 17.7 \text{ V}$$

$$V_{right} = I_{tot} R_{right} = 7.38 \cdot 4.1 = 30.3 \text{ V}$$

$$I_{12} = \frac{17.7}{12} = 1.48 \text{ A}$$

$$I_3 = \frac{17.7}{3} = 5.90 \text{ A}$$


$$I_6 = \frac{30.3}{6} = 5.05 \text{ A}$$

$$I_{13} = \frac{30.3}{13} = 2.33 \text{ A}$$

To find the current through the switch, we need to apply Kirchhoff's junction rule at either a or b. At a: $I_{12} + I_{switch} = I_6$ and at b: $I_3 = I_{switch} + I_{13}$. Either way, we see that the current through the switch is directed up with a value


$$I_{switch} = I_6 - I_{12} = I_3 - I_{13} = 5.05 - 1.48 = 5.90 - 2.33 = 3.57 \text{ A}$$

3. In the circuit below solve for

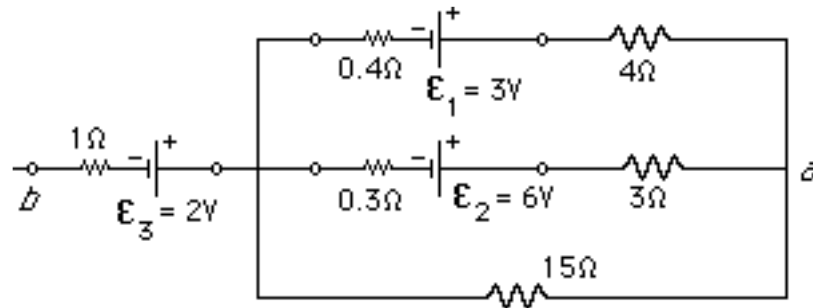

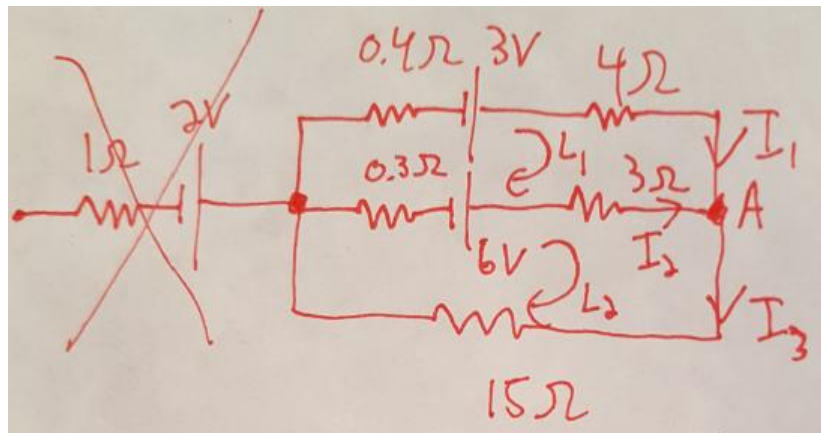(a) the current in each part of the circuit,

Note that the question specifies this is an entire circuit, not a section of circuit. On the far left, the branch ends at b and does not form any closed loop, meaning there is no current in this branch and the emf $\mathcal{E}_3$ does not send any power to the rest of the circuit. We can simply ignore this far left branch in our analysis.



I've chosen to define currents I_1 , I_2 and I_3 as shown above. Applying Kirchhoff's rules:

$$\text{Junction: } I_1 + I_2 = I_3$$

$$\text{Top loop: } +3 - 4I_1 + 3I_2 - 6 + 0.3I_2 - 0.4I_1 = 0 = -3 - 4.4I_1 + 3.3I_2$$

$$\text{Bottom loop: } +6 - 3I_2 - 15I_3 - 0.3I_2 = 0 = 6 - 3.3I_2 - 15I_3$$

$$\text{Outside loop: } +3 - 4I_1 - 15I_3 - 0.4I_1 = 0 = 3 - 4.4I_1 - 15I_3$$

We only need two of the three loop equations to solve. I'll use the top loop to isolate I_1 in terms of I_2 and the bottom loop to isolate I_3 in terms of I_2 . Then, we substitute into the junction equation:

$$I_1 = \frac{-3 + 3.3I_2}{4.4}$$

$$I_3 = \frac{6 - 3.3I_2}{15}$$

$$I_2 = I_3 - I_1 = \left(\frac{6 - 3.3I_2}{15} \right) - \left(\frac{-3 + 3.3I_2}{4.4} \right) = 1.08 - 0.97I_2$$

We can now find the three currents:

$$I_2 = \frac{1.08}{1.97} = 0.548 \text{ A (to the right)}$$

$$I_1 = \frac{-3 + 3.3 \cdot 0.548}{4.4} = -0.271 \text{ A (opposite the initial guess, so to the left)}$$

$$I_3 = \frac{6 - 3.3 \cdot 0.548}{15} = 0.279 \text{ A (to the left)}$$

4

(b) the potential difference V_{ab} ,

We can use any of the three branches to find V_{ab} , being careful not to forget $\mathcal{E}_3$.

$$\text{Top: } V_b + \mathcal{E}_3 - 4.4I_1 + \mathcal{E}_1 = V_a$$

$$\text{Middle: } V_b + \mathcal{E}_3 - 3.3I_2 + \mathcal{E}_2 = V_a$$

$$\text{Bottom: } V_b + \mathcal{E}_3 + 15I_3 = V_a$$

In all cases,

$$V_a - V_b = 2 - 4.4 \cdot (-0.271) + 3 = 2 - 3.3 \cdot 0.548 + 6 = 2 + 15 \cdot 0.279 = 6.19 \text{ V}$$

(b) the terminal voltage of the seat $\mathcal{E}_1$, and

The terminal voltage of the seat $\mathcal{E}_1$ includes its internal resistance of 0.4Ω .

$$V_T = -0.4I_1 + \mathcal{E}_1 = (-0.4)(-0.271) + 3 = 3.11 \text{ V}$$

(d) the rate at which this seat supplies/absorbs electrical energy.


This seat has current going through it “backwards”, so it **absorbs** electrical energy at a rate

$$P = I_1 V_T = (-0.271)(3.11) = -0.84 \text{ W}$$

We could of course sum the power of the emf and the resistance separately:


$$|P| = |I_1 \mathcal{E}_1| + |I_2 r_1| = (0.271)(3) + (0.271)^2(0.4) = 0.84 \text{ W}$$

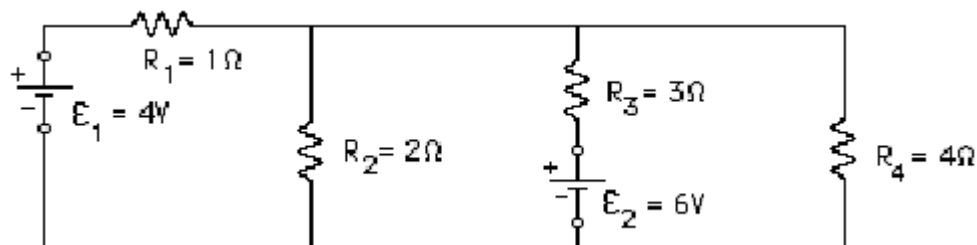4. For the circuit shown in the figure below, determine the current through each resistor



Before applying Kirchhoff's rules, we can simplify the circuit by replacing R_2 and R_4

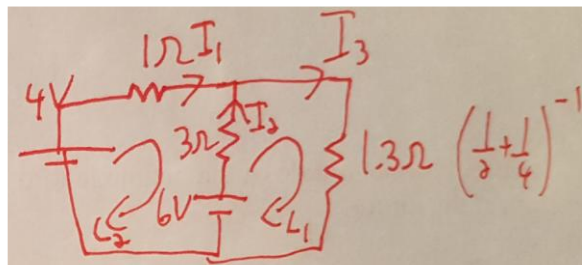connected in parallel, themselves parallel to the rest of the circuit. $R_{24} = \left(\frac{1}{2} + \frac{1}{4}\right)^{-1} = 1.33 \Omega$



I've chosen to define currents I_1 , I_2 and I_3 as shown above. Applying Kirchhoff's rules:

$$\text{Junction: } I_1 + I_2 = I_3$$

$$\text{Left loop: } +4 - 1I_1 + 3I_2 - 6 = 0 = -2 - I_1 + 3I_2$$

$$\text{Right loop: } +6 - 3I_2 - 1.33I_3 = 0$$

$$\text{Outside loop: } +4 - 1I_1 - 1.33I_3 = 0$$

We only need two of the three loop equations to solve. I'll use the left loop to isolate I_1 in terms of I_2 and the right loop to isolate I_3 in terms of I_2 . Then, we substitute into the junction equation:

$$I_1 = -2 + 3I_2$$

$$I_3 = \frac{6-3I_2}{1.33}$$

$$I_2 = I_3 - I_1 = \left(\frac{6-3I_2}{1.33}\right) - (-2 + 3I_2) = 8 - 5.26I_2$$

We can now find the three currents:

$$I_2 = \frac{8}{6.26} = 1.28 \text{ A (up, this is the current through } R_3)$$

$$I_1 = -2 + 3 \cdot 1.28 = 1.84 \text{ A (up, so to the right through } R_1)$$

$$I_3 = \frac{6-3 \cdot 1.28}{1.33} = 1.62 \text{ A (down, so this is the sum of the currents through } R_2 \text{ and } R_4)$$

To find the current through R_2 and R_4 , we must find the voltage drop across them. This can be done with Ohm's law or with the voltage loops, with small differences from rounding:


$$V_{24} = I_3 R_{24} = 1.62 \cdot 1.33 = 2.15 \text{ V}$$

$$V_{24} = \mathcal{E}_1 - I_1 R_1 = 4 - 1.84 \cdot 1 = 2.16 \text{ V}$$

$$V_{24} = \mathcal{E}_2 - I_2 R_3 = 6 - 1.28 \cdot 3 = 2.16 \text{ V}$$

Through R_2 , $I = \frac{2.16}{2} = 1.08 \text{ A}$ and through R_4 , $I = \frac{2.16}{4} = 0.54 \text{ A}$, both downwards.

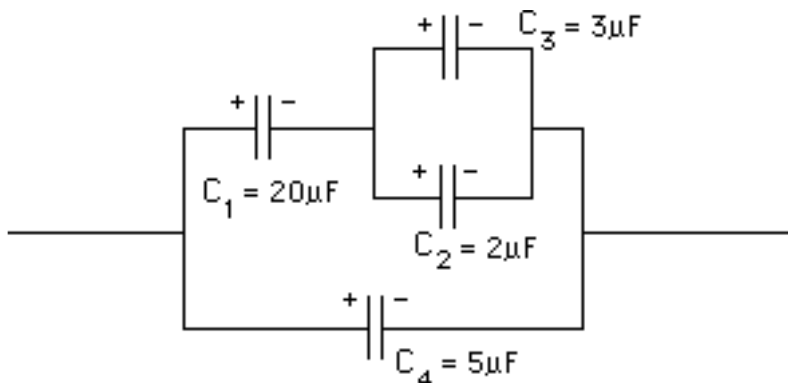5. In the combination of capacitors shown below, all are fully charged.



(a) Determine the equivalent capacitance of the combination.

First, C_2 and C_3 are connected in parallel, so $C_{23} = 2 + 3 = 5 \mu\text{F}$. These are connected to C_1 in series, so $C_{123} = \left(\frac{1}{20} + \frac{1}{5}\right)^{-1} = 4 \mu\text{F}$. This is finally in parallel with C_4 , so $C_{eq} = 4 + 5 = 9 \mu\text{F}$.

(b) If the charge on C_3 is $90 \mu\text{C}$, determine the charge on C_4 .


Since we know the charge on C_3 , we can find the voltage across it $V_3 = \frac{Q_3}{C_3} = \frac{90 \times 10^{-6}}{3 \times 10^{-6}} = 30 \text{ V}$.

This is also the voltage across C_2 : $V_3 = V_2 = V_{23} = 30 \text{ V}$. We can find the charge on C_2 and C_3 with their equivalent capacitance C_{23} : $Q_{23} = C_{23} V_{23} = 5 \cdot 30 = 150 \mu\text{C}$.

This is also the charge on C_1 : $Q_1 = Q_{23} = Q_{123} = 150 \mu\text{C}$. We can now find the voltage across C_1 , C_2 and C_3 : $V_{123} = \frac{Q_{123}}{C_{123}} = \frac{150}{4} = 37.5 \text{ V}$.

This is also the voltage across C_4 : $V_4 = V_{123} = V_{tot}$. Finally, we can find the charge on C_4 : $Q_4 = C_4 V_4 = 5 \cdot 37.5 = 188 \mu\text{C}$

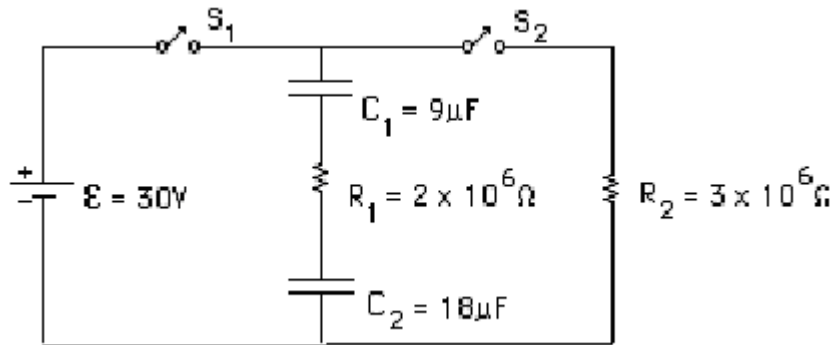6. In the circuit shown below the switches S_1 and S_2 are initially open and the capacitors are uncharged.



(a) Switch S_1 is now closed. Six seconds after S_1 is closed :

(i) what is the charge on C_1 ?

C_1 and C_2 are connected in series, so $C_{eq} = \left(\frac{1}{9} + \frac{1}{18}\right)^{-1} = 6 \mu\text{F}$. The time constant of the circuit is thus $\tau = R_{eq} C_{eq} = (2 \times 10^{-6})(6 \times 10^{-6}) = 12 \text{ s}$.

The maximum charge that can be accumulated on the capacitors (equal charge on C_1 and C_2 as they are in series) is $Q_{max} = C_{eq} \mathcal{E} = 6 \times 30 = 180 \mu\text{F}$.

This charge increases over times as $Q(t) = Q_{max} \left(1 - e^{-\frac{t}{\tau}}\right)$

$$Q(t = 6\text{s}) = 180 \left(1 - e^{-\frac{6}{12}}\right) = 70.8 \mu\text{C}$$

(ii) what is the current through R_1 ?

We could find the initial current through R_1 and then find $I(t) = I_{max} e^{-\frac{t}{\tau}}$.

Instead, since we already know the accumulated charge, we know that the voltage across the capacitors is $V_C = \frac{Q(t)}{C_{eq}} = \frac{70.8}{6} = 11.8 \text{ V}$.

The voltage across the resistor is thus $V_R = \mathcal{E} - V_C = 30 - 11.8 = 18.2 \text{ V}$, and the current through it is $I(t = 6\text{s}) = \frac{V_R}{R} = \frac{18.2}{2 \times 10^6} = 9.10 \mu\text{A}$

(iii) what is the electric potential energy stored in C_2 ?

No need to find the voltage across only C_2 , since we know its capacitance and

$$\text{charge. } U = \frac{Q^2}{2C} = \frac{(70.8 \times 10^{-6})^2}{2(18 \times 10^{-6})} = 1.39 \times 10^{-4} \text{ J.}$$

(b) **If now, at six seconds after switch S_1 has been closed, it is opened and S_2 is closed.**

(i) Determine the charge on C_2 18 seconds after S_2 is closed and

The discharging circuit has a new time constant

$$\tau = R_{eq}C_{eq} = (3 \times 10^{-6})(6 \times 10^{-6}) = 18 \text{ s}$$

The charge on C_2 is the same as on C_1 and begins as $Q_{max} = 70.8 \text{ } \mu\text{C}$ and then

$$\text{decreases over time: } Q(t) = Q_{max}e^{-\frac{t}{\tau}}$$

$$Q(t = 18 \text{ s}) = 70.8 e^{-18/18} = 26.0 \text{ } \mu\text{C}$$

(ii) determine the potential difference across R_2 at this time.

In this discharging circuit, the voltage across R_2 is the same as over the two capacitors together

$$V_R = V_{C_{eq}} = \frac{Q(t)}{C_{eq}} = \frac{26.0}{6} = 4.33 \text{ V}$$